

Automotive Electrical Systems


Basic Electricity

Donald Jones
Brookhaven College

Automotive Electrical Systems

What is Electricity?

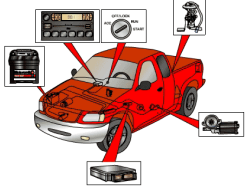
- Electricity is the flow of charges through a conductor
- This flow of charges can be used to generate heat, light or magnetism
- List several specific automotive applications of electricity



Automotive Electrical Systems

Elements


- An element is composed of one type of atom
- There are over a 100 different elements in the Periodic Table of Elements
- The number of protons in an atom determines its atomic number



Automotive Electrical Systems

Atomic Structure

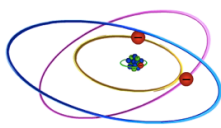
- Protons
 - Positive charge
 - Located in nucleus
- Neutrons
 - Neutral charge
 - Acts as the glue holding protons in the nucleus together
- Electrons
 - Negative charge
 - Orbit the nucleus



Automotive Electrical Systems

Electron Shells

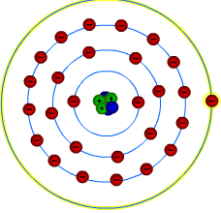
- $2n^2$ rule
- First shell – K
 - 2 electrons
- Second shell – L
 - 8 electrons
- Third shell – M
 - 18 electrons
- Fourth shell – N
 - 32 electrons



Automotive Electrical Systems

Valence Shells

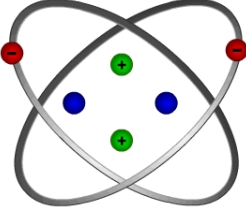
- An atom's outer most ring or shell is referred to as its valence ring
- The number of electrons in the valence ring determines if a material is a
 - Conductor
 - Insulator
 - Semiconductor



Automotive Electrical Systems

Conductors and Insulators

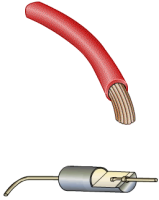
- **Conductor**
 - Materials with three or less electrons in the valence shell
- **Insulator**
 - Materials with 5 or more electrons in the valence shell
- **Semiconductor**
 - Materials with four electrons in the valence shell



Automotive Electrical Systems

Conductor Characteristics

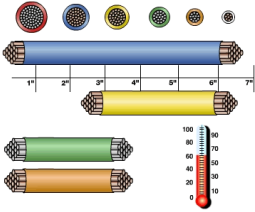
- A conductor's resistance is influenced by:
 - Atomic structure
 - Length
 - Diameter
 - Temperature
 - Condition



Automotive Electrical Systems

Semiconductors

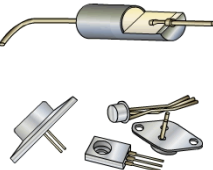
- Semiconductors have exactly four electrons in their valence shell
- Semiconductors only conduct electricity under very specific conditions
- Diodes and transistors are examples of semiconductors



Automotive Electrical Systems

Basic Electricity

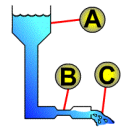- **Electrical Pressure**
 - voltage
 - measured in volts
- **Current Flow**
 - amperage
 - measured in amps
- **Opposition to Current Flow**
 - resistance
 - measured in ohms




A - voltage
B - resistance
C - amperage

Automotive Electrical Systems

AC and DC Current

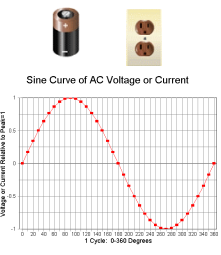- Direct current flows in a single direction, from positive to negative
- Alternating current changes directions from positive to negative many times a second



Sine Curve of AC Voltage or Current


Wave of Current Relative to Inverse

1 Cycle: 360 Degrees

Automotive Electrical Systems

Circuit Components

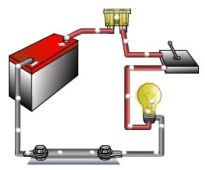
- Power Source
- Conductor
- Load
- Switch
- Circuit Protection



Automotive Electrical Systems

Circuit Voltage

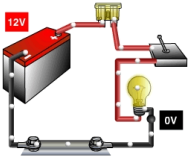
- Voltage is dropped across each load in a circuit
- A voltage drop occurs only when current is flowing
- Voltmeters measure the difference in electrical pressure between two points in a circuit



Automotive Electrical Systems

Ohm's Law

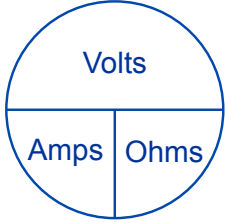
- $V = A \times O$
- $A = V / O$
- $O = V / A$



Automotive Electrical Systems

Applying Ohms Law

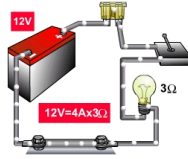
- $V_S = I_T \times R_T$
- $12V = 4A \times 3\Omega$
- How will low battery voltage impact cranking speed?



Automotive Electrical Systems

Series Circuit

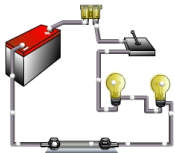
- One path for current flow
- Total circuit resistance is the sum of all the circuit's resistances
- The sum of the voltage drops equals source voltage



Automotive Electrical Systems

Series Circuit Resistance

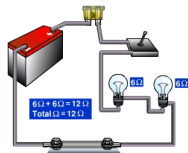
- $R_T = R_1 + R_2 \dots$
- $6\Omega + 6\Omega = 12\Omega$
- Increasing the number of loads in a series circuit increases the circuit's resistance



Automotive Electrical Systems

Series Circuit Current Flow

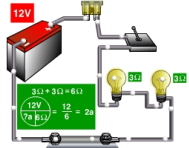
- $V_S = 12V$
- Calculate R_T
 - $R_T = R_1 + R_2 \dots$
 - $3\Omega + 3\Omega = 6\Omega$
- $I_T = V_S / R_T$
 - $12V / 6\Omega = 2A$
- What would happen to the current flow if resistance increased?



Automotive Electrical Systems

Series Circuit Calculations

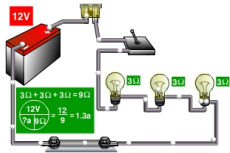
- $R_T = R_1 + R_2 \dots$
 - $3\Omega + 3\Omega + 3\Omega = 9\Omega$
- $I_T = V_S / R_T$
 - $12V / 9\Omega = 1.3A$
- What happens to the bulbs' intensity as compared to the previous circuit?



Automotive Electrical Systems

Series Circuit Voltage Drops

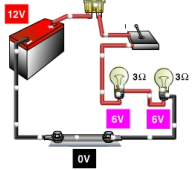
- Voltage drops may be calculated by multiplying the load's resistance by the current flowing through the load or:
 - $V_D R_x = R_x \times I_T$
- $R_T = R_1 + R_2 \dots$
 - $3\Omega + 3\Omega = 6\Omega$
- $I_T = V_S / R_T$
 - $12V / 6\Omega = 2A$
- $V_D R_1 = R_1 \times I_T$
 - $6V = 2A \times 3\Omega$



Automotive Electrical Systems

Parallel Circuits

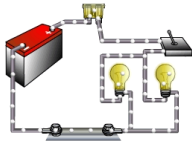
- There are multiple paths for current flow
- Source voltage is dropped across each path
- Total current is equal to the sum of current flowing through all the branches
- Total circuit resistance is always less than the least resistive branch



Automotive Electrical Systems

Parallel Circuit Calculations

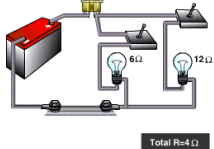- Source voltage is dropped across each load
- $I_T = (V_S / R_1) + (V_S / R_2)$
 - $3A = (12V / 6\Omega) + (12V / 12\Omega)$
- $R_T = V_S / I_T$
 - $12V / 3A = 4\Omega$
- What happens to a parallel circuit's resistance if additional loads are added?



Automotive Electrical Systems

Digital Volt Ohm Meters

- Display
 - number of digits
 - V, A or Ω
 - units indicator
- Range Selection
 - auto-ranging
 - manual operation
- Test Lead Connection



Automotive Electrical Systems


Units of Measurement

- mega - M
 - multiply meter reading by 1,000,000
- kilo - k
 - multiply meter reading by 1,000
- milli - m
 - multiply meter reading by .001
- micro - μ
 - multiply meter reading by .000001

Automotive Electrical Systems

Meter Operation


- Voltage drop must be measured with the current flowing
- An ammeter must be in series with the circuit being tested
- An ohmmeter should be used only with the circuit or component removed from the circuit (no power applied)



Automotive Electrical Systems

Measuring Voltage

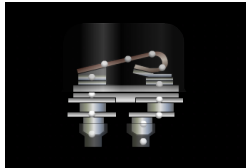
- Be certain the leads are connected correctly
- Select the correct scale if the meter is not auto-ranging
- Connect the leads to the component being tested
- Current must be flowing to measure voltage drop



Automotive Electrical Systems

Continuity Tests

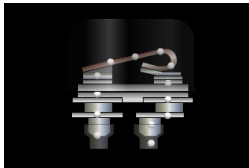- Always isolate the circuit you are testing for continuity
- A meter reading of OL indicates no continuity
- A numeric reading indicates continuity although it may not be desired or within specifications



Automotive Electrical Systems

Shorts and Opens

- Short
 - unwanted continuity exists between two or more circuits
 - the meter displays a resistance less than specifications
- Open
 - the desired continuity between two points in a circuit is not present
 - the meter shows OL

