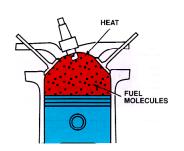



Spark Quality

- Heat to ignite fuel molecules
- Duration to last long enough so the the combustion process is started properly




Heat




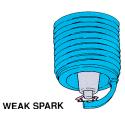


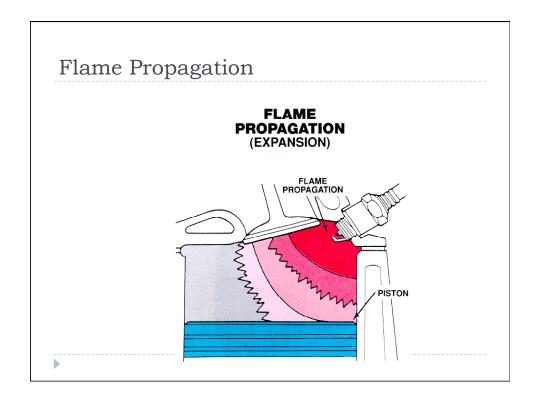
- Heat generated by electrons jumping a air gap
- More electrons hotter spark or more heat
- Less electrons weaker spark or less heat



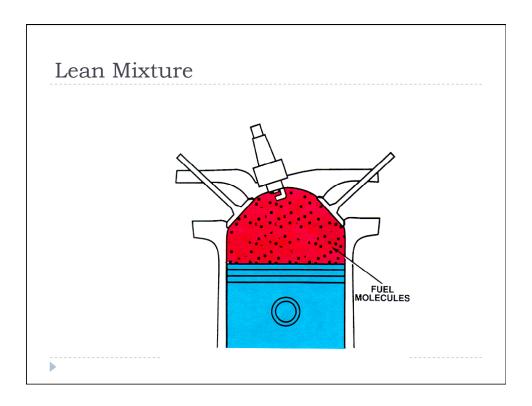Spark Duration Length of time spark is maintained Measured in Milliseconds (ms) Typically between .8 and 1.5 ms Needs to be long enough to allow proper Flame propagation



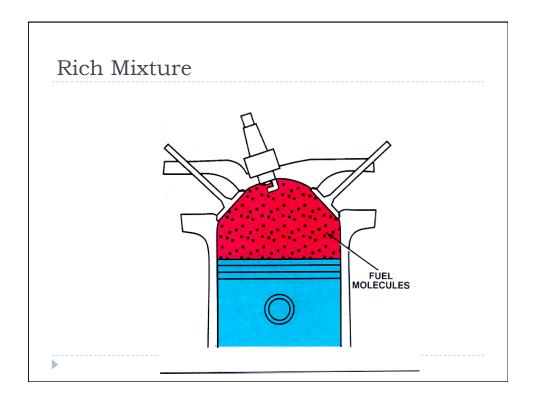


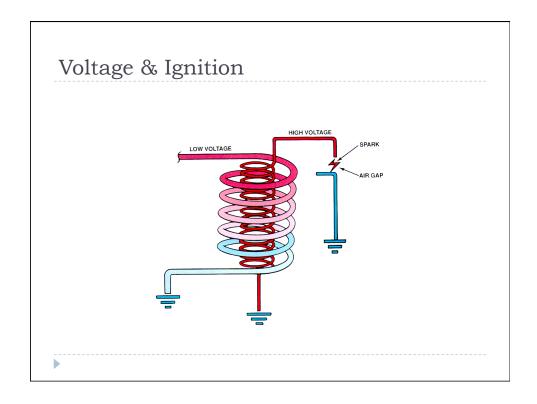


Ignition System Theory & Operation Basic Ignition


Ignition Coil

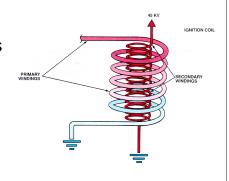
- Converts low voltage to high voltage
- > Start with 12 14 volts
- ▶ Produce up to 40 Kv
- Typically work in the 20 - 25 Kv range




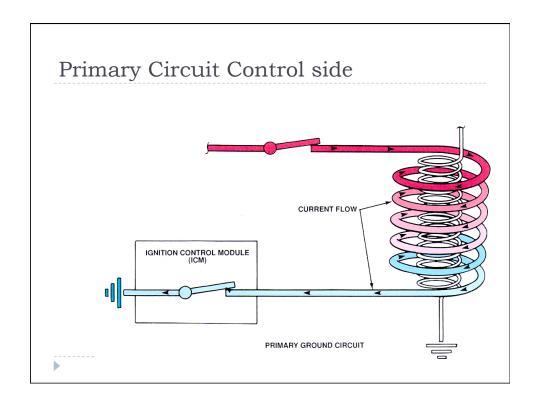
Primary Circuit Supply Side B+ (12V) PRIMARY WINDINGS




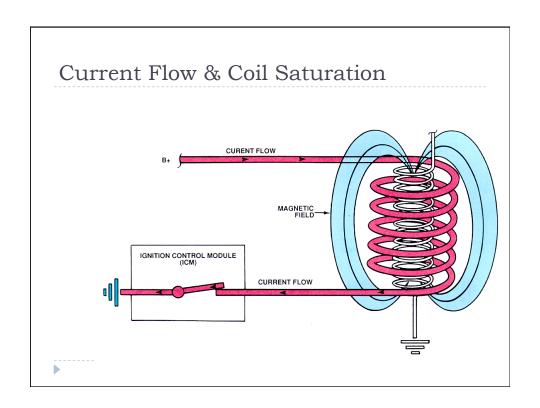


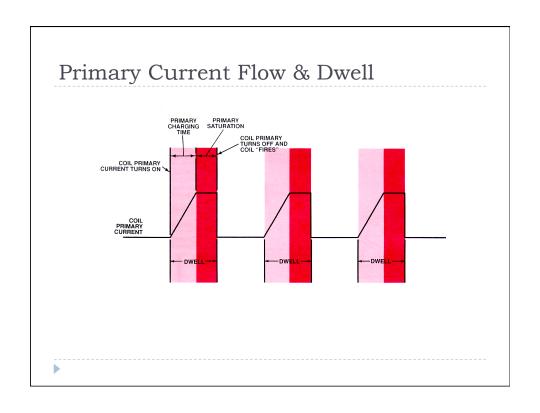


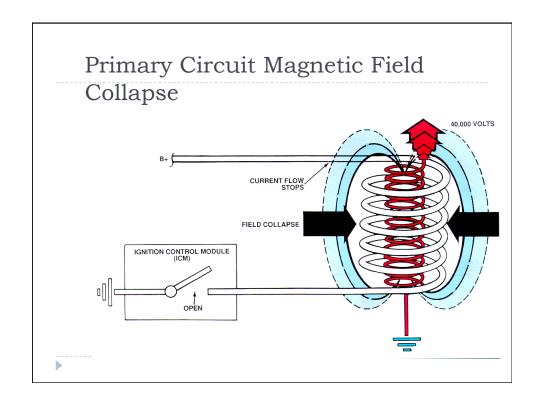


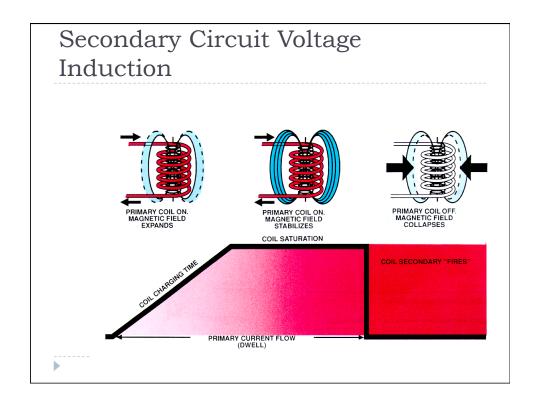


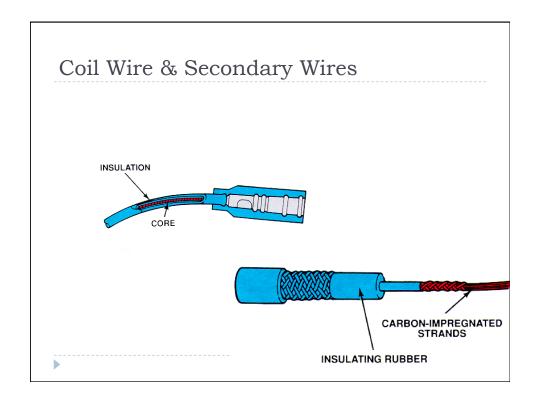


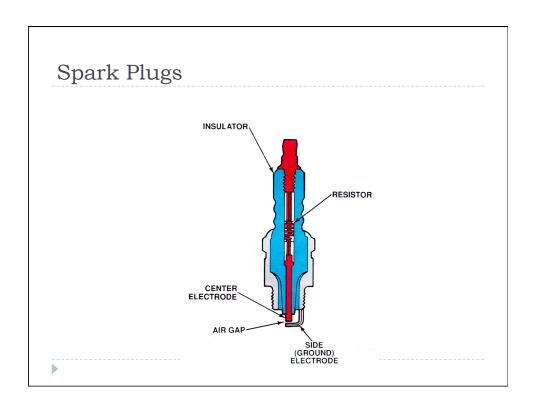


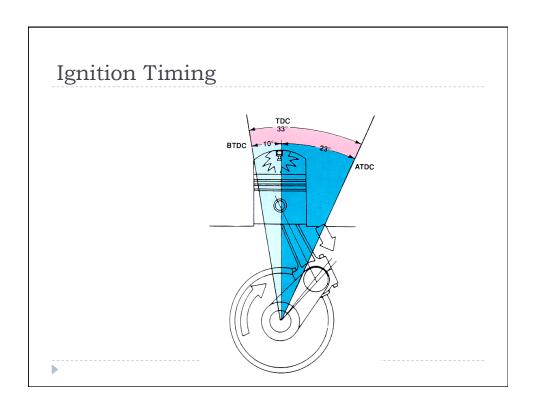


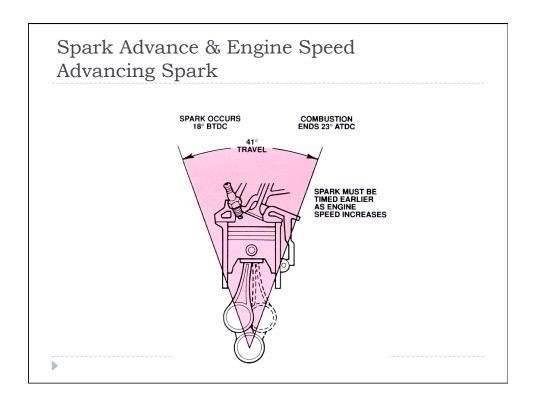


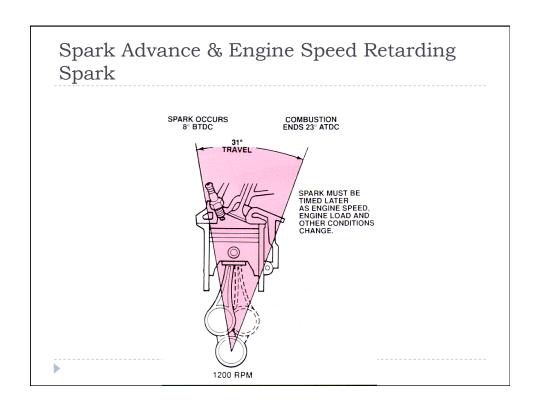


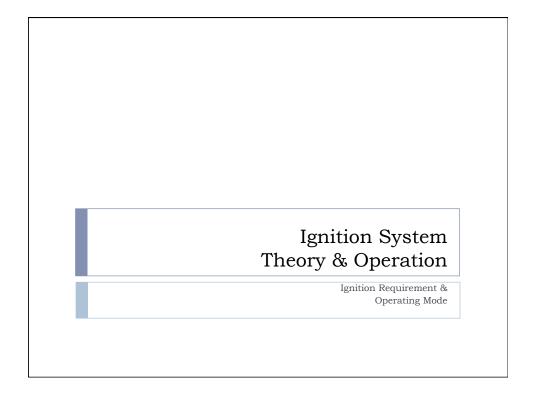


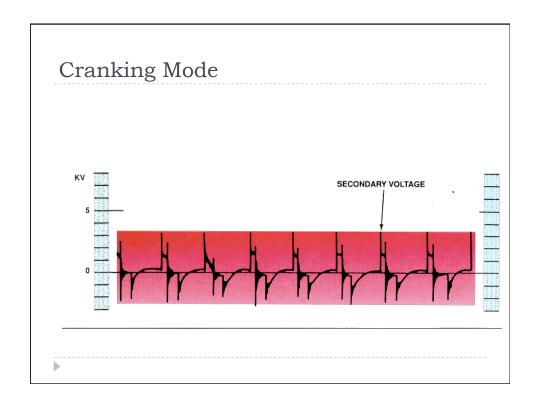

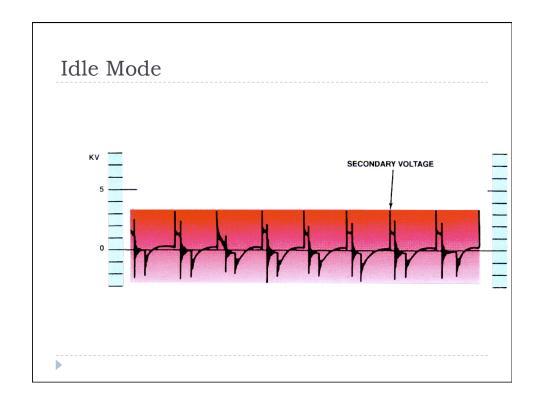

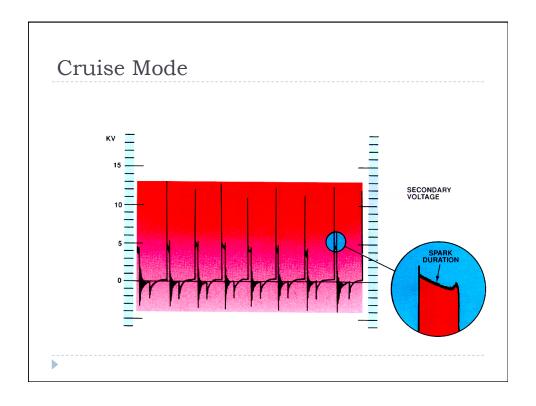

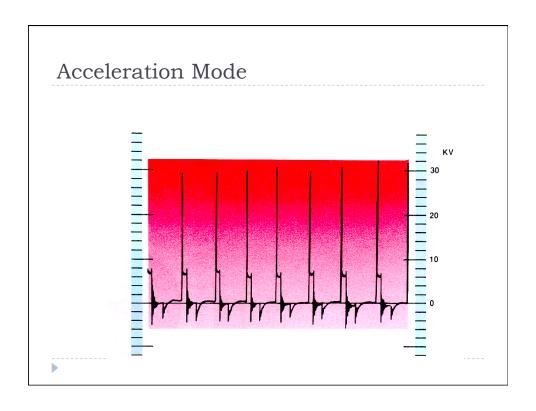

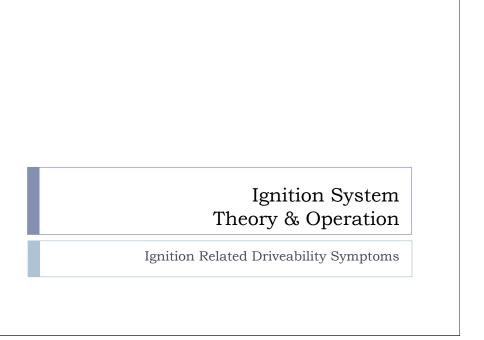


Ignition Conditions


- ▶ No spark
- ▶ Loss of spark
- Weak spark
- Improper timing

No Spark

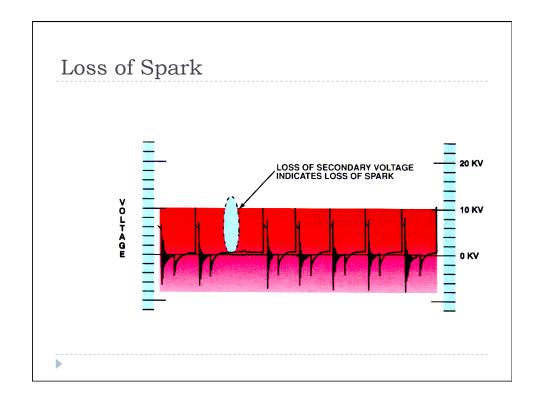
- No spark present at the spark plugs could easily be found with a simple spark tester.
- A No Spark situation can be caused by no power applied to coil/s no crankshaft position sensor signal or no commanded ground from the module.
- If spark is not available on a single spark plug the cause may be due to faulty COP coil, spark plug wire, or cap/ rotor issue.





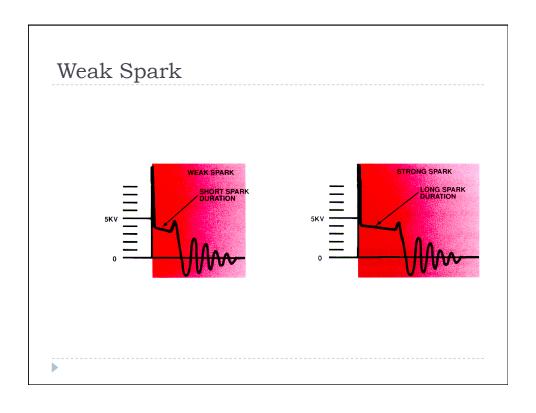

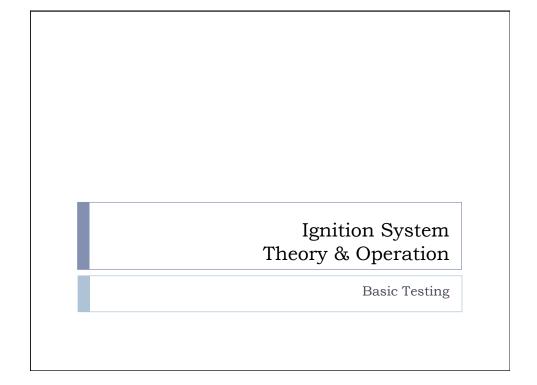Symptoms & Conditions CONDITIONS No Spark Loss of Spark Weak Spark Timing No Start Hard Start Quits After Start Stalls Idle-Fast/slow Misses/Rough Run Buck/Jerk Stumble Induction Backfire Loss of Power Spark Knock Poor Fuel Economy* Excessive Emissions* * In most instances other symptoms will be present.



Primary Circuit Tests



- ▶ General circuit tests
- ▶ Coil supply voltage
- Coil primary circuit ground
- ▶ Coil primary resistance
- Coil dwell- saturation

TFI IV Coil




EI Coil





Coil On Plug




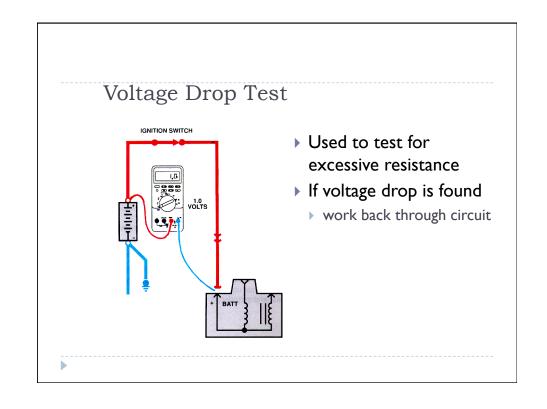Voltage Supply Test Ney on Battery voltage to coil positive terminal No power check circuit back through connector and ignition switch



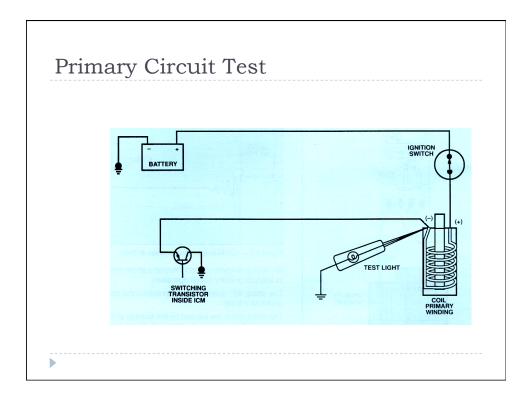

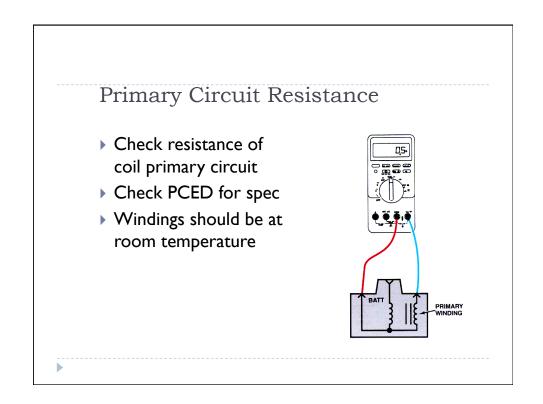


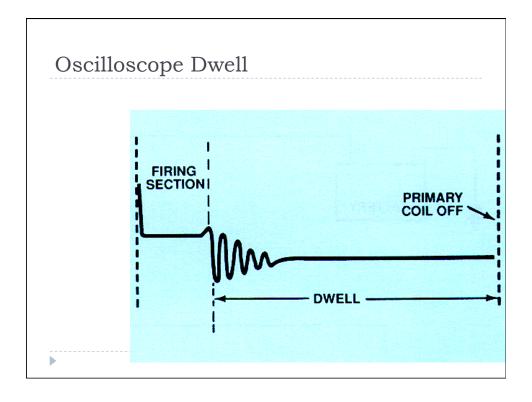



Secondary Circuit Tests

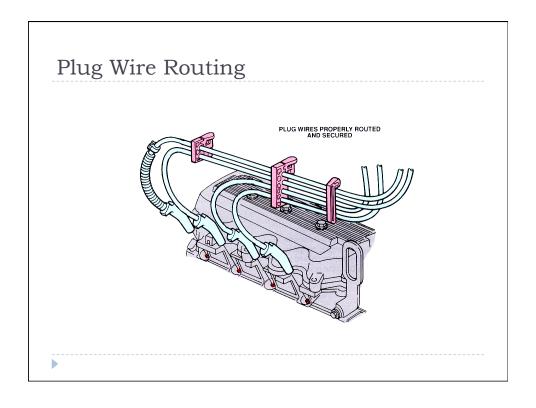
- ▶ General circuit condition
- ▶ Coil secondary resistance
- Secondary wire resistar
- Secondary required vol-
- ▶ Spark duration
- ▶ Plug condition







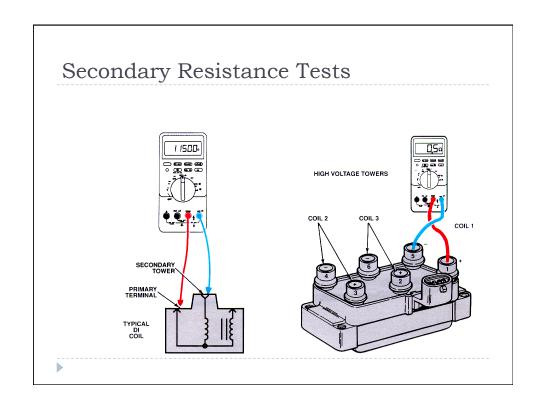


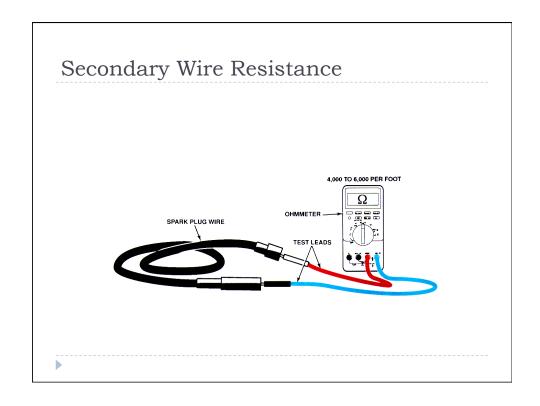


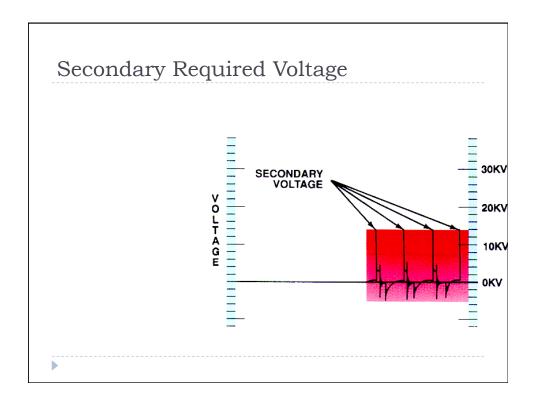


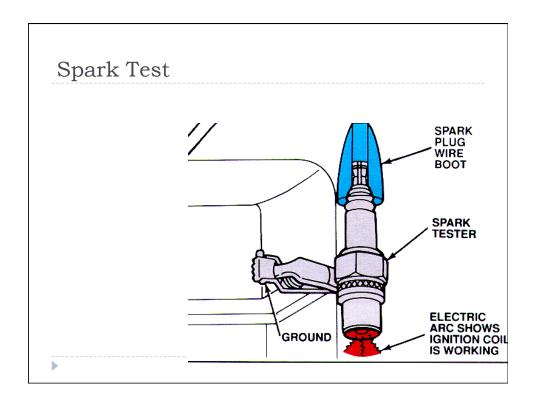


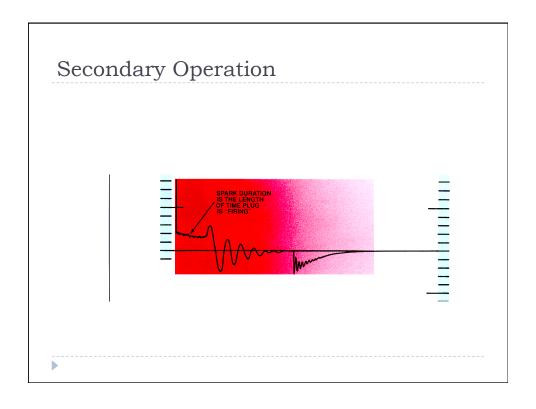


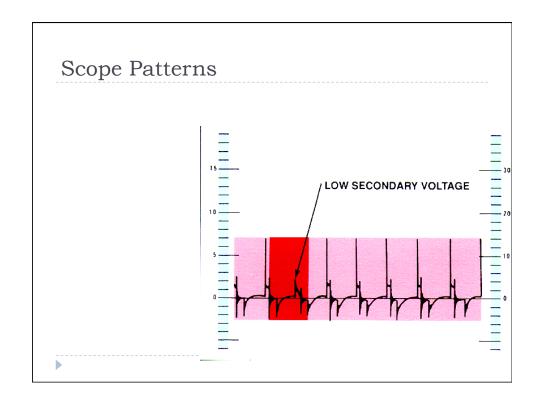


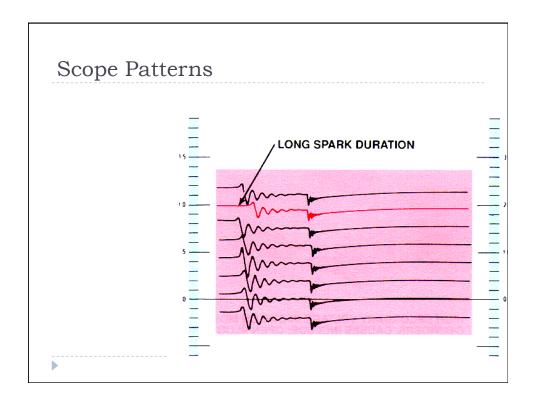

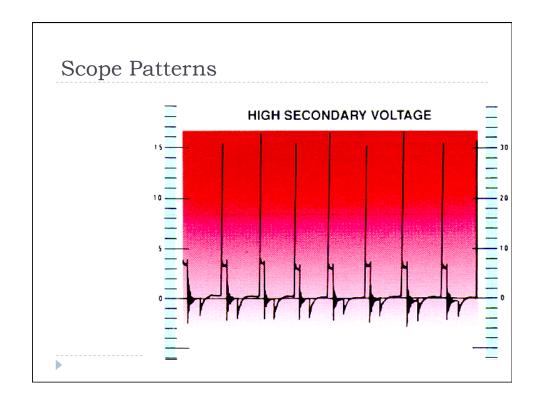

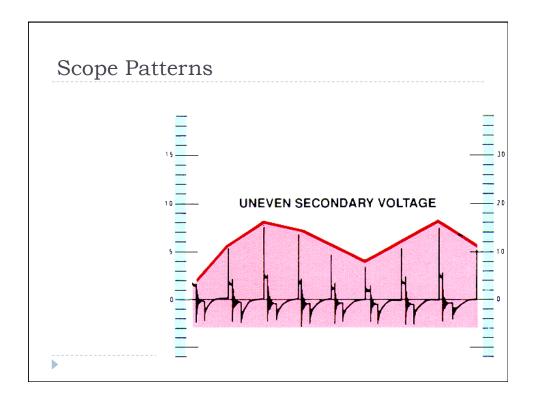

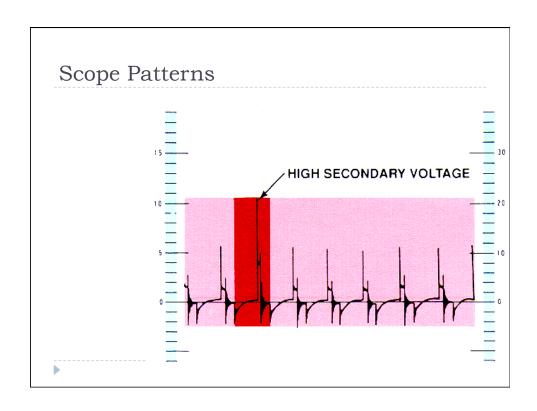

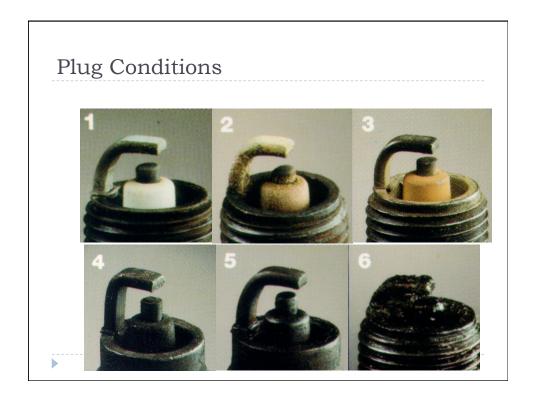

Plug Conditions



Plug Air Gap

▶ IMPORTANT!

- Narrow
 - ▶ long duration
 - ▶ low voltage
- Wide
 - ▶ short duration
 - ▶ higher voltage

